

INL/DNL analysis of current steering DAC

Relative matching ("coefficient of variation")

$$\begin{cases} \sigma_u \stackrel{\text{def}}{=} \frac{\sigma}{\mu} = \text{stdev}\left(\frac{\Delta I}{I}\right) \\ I_j \stackrel{\text{def}}{=} I + \Delta I \end{cases}$$

1.1 INL of thermometer DAC

$$\begin{cases} INL(k) = \frac{I_{out}(k) - I_{out,uniform}(k)}{Step_{avg}} = \frac{\sum_{j=1}^k I_j - \frac{k}{N} \sum_{j=1}^N I_j}{\frac{1}{N} \sum_{j=1}^N I_j} = N \cdot \frac{\sum_{j=1}^k I_j}{\sum_{j=1}^N I_j} - k = N \cdot \frac{\sum_{j=1}^k I_j}{\sum_{j=1}^k I_j + \sum_{j=k+1}^N I_j} - k \\ A \stackrel{\text{def}}{=} \sum_{j=1}^k I_j, B \stackrel{\text{def}}{=} \sum_{j=k+1}^N I_j \end{cases}$$

$$\xrightarrow{\text{yields}} INL(k) = N \cdot \frac{A}{A+B}$$

$$Var(INL(k)) = Var\left(N \cdot \frac{A}{A+B}\right) = N^2 \cdot Var\left(\frac{A}{A+B}\right) \xrightarrow{X=A, Y=A+B} N^2 \cdot Var\left(\frac{X}{Y}\right)$$

Note A and B is independent, but X and Y is dependent.

Because

$$\begin{aligned} Var\left(\frac{X}{Y}\right) &= \left(\frac{\mu_X}{\mu_Y}\right)^2 \left(\frac{\sigma_X^2}{\mu_X^2} + \frac{\sigma_Y^2}{\mu_Y^2} - 2 \frac{COV(X,Y)}{\mu_X \mu_Y}\right) \\ \begin{cases} \left(\frac{\mu_X}{\mu_Y}\right)^2 &= \frac{k^2}{N^2} \\ \frac{\sigma_X^2}{\mu_X^2} &= \frac{1}{k} \frac{\sigma^2}{I^2}, \frac{\sigma_Y^2}{\mu_Y^2} = \frac{1}{N} \frac{\sigma^2}{I^2} \\ COV(X,Y) &= E(XY) - E(X)E(Y) = E(A(A+B)) - kI \cdot NI = E(A^2) + E(AB) - Nk \cdot I^2 \\ &= Var(A) + E(A)^2 + E(A)E(B) - Nk \cdot I^2 \\ &= k \cdot \sigma^2 + k^2 I^2 + k(N-k)I^2 - Nk \cdot I^2 \\ &= k \cdot \sigma^2 \end{cases} \\ \xrightarrow{\text{yields}} Var\left(\frac{X}{Y}\right) &= \frac{k^2}{N^2} \left(\frac{1}{k} - \frac{1}{N}\right) \frac{\sigma^2}{I^2} \end{aligned}$$

Then,

$$Var(INL(k)) = N^2 \cdot \frac{k^2}{N^2} \left(\frac{1}{k} - \frac{1}{N}\right) \frac{\sigma^2}{I^2} = k \left(1 - \frac{k}{N}\right) \frac{\sigma^2}{I^2}$$


So,

$$\sigma_{INL,k} = \sqrt{k \left(1 - \frac{k}{N}\right)} \cdot \frac{\sigma}{I} = \sqrt{k \left(1 - \frac{k}{N}\right)} \cdot \sigma_u$$

Worst case $k = N/2$

$$\sigma_{INL,max} \approx \frac{1}{2} \sigma_u \sqrt{2N}$$
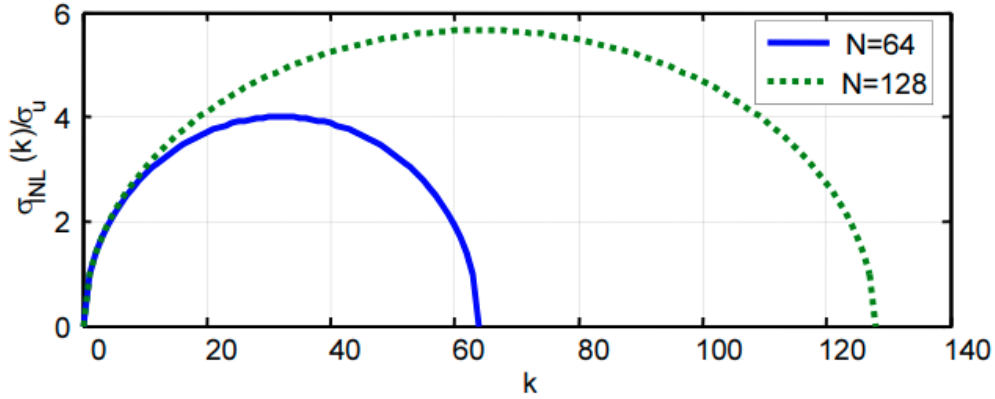
$$B = 2 + 2\log_2\left(\frac{\sigma_{INL}}{\sigma_u}\right)$$



1.2 DNL of thermometer DAC

$$\begin{cases} DNL(k) = \frac{Step(k) - Step_{avg}}{Step_{avg}} \\ Step_{avg} = \frac{1}{N} \sum_{j=1}^N I_j \end{cases} \xrightarrow{\text{yields}} DNL(k) = \frac{I_k - \frac{1}{N} \sum_{j=1}^N I_j}{\frac{1}{N} \sum_{j=1}^N I_j}$$

$$DNL(k) = \frac{I + \Delta I_k - \frac{1}{N} \sum_{j=1}^N (I + \Delta I_j)}{\frac{1}{N} \sum_{j=1}^N (I + \Delta I_j)} = \frac{\left(1 - \frac{1}{N}\right) \Delta I_k - \frac{1}{N} \sum_{j=1; j \neq k}^N \Delta I_j}{I + \frac{1}{N} \sum_{j=1}^N \Delta I_j} \xrightarrow{\text{ommit } \frac{1}{N} \sum_{j=1}^N \Delta I_j}$$

$$DNL(k) = \frac{\left(1 - \frac{1}{N}\right) \Delta I_k - \frac{1}{N} \sum_{j=1; j \neq k}^N \Delta I_j}{I} = \left(1 - \frac{1}{N}\right) \frac{\Delta I_k}{I} - \frac{1}{N} \sum_{j=1; j \neq k}^N \frac{\Delta I_j}{I}$$

$$Var(DNL(k)) = \left[\left(1 - \frac{1}{N}\right)^2 + \frac{N-1}{N^2} \right] \frac{\sigma^2}{I^2} = \frac{N-1}{N} \frac{\sigma^2}{I^2} \xrightarrow{\text{yields}}$$

$$\sigma_{DNL,k} = \sqrt{1 - \frac{1}{N} \cdot \frac{\sigma}{I}} = \sqrt{1 - \frac{1}{N}} \sigma_u \xrightarrow{N \gg 1}$$

$$\sigma_{DNL,k} = \sigma_u$$

Another approximation method

$$DNL(k) = \frac{Step(k) - Step_{avg}}{Step_{avg}} = \frac{I + \Delta I - I}{I} = \frac{\Delta I}{I}$$

$$\sigma_{DNL,k} = stdev\left(\frac{\Delta I}{I}\right) = \sigma_u$$

2.1 INL of Binary Weighted DAC

INL same as for thermometer DAC

2.2 DNL of Binary Weighted DAC

Assume $X_{[1,k]} \cap Y_{[1,k-1]} = \emptyset$

$$\begin{cases} DNL(k) = \frac{Step(k) - Step_{avg}}{Step_{avg}} \\ Step(k) = \sum_{i=1}^k X_i - \sum_{j=1}^{k-1} Y_j \end{cases} \xrightarrow{\text{yields}}$$

$$DNL(k) = \sum_{i=1}^k \frac{X_i - Step_{avg}}{Step_{avg}} - \sum_{j=1}^{k-1} \frac{Y_j - Step_{avg}}{Step_{avg}} = \sum_{i=1}^k DNL, th, i - \sum_{j=1}^{k-1} DNL, th, j$$

DNL, th, i is given by thermometer DNL formula, so

$$Var(DNL(k)) = (k + k - 1) \cdot \left(\sqrt{1 - \frac{1}{N}} \sigma_u \right)^2$$

$$\sigma_{DNL,k} = \sqrt{2k-1} \sqrt{1 - \frac{1}{N}} \sigma_u \xrightarrow{N \gg 1} \sqrt{2k-1} \sigma_u$$


Worst case@ $k = 2^{B-1}, k-1 = 2^{B-1} - 1$

$$\sigma_{DNL,k} = \sqrt{2^B - 1} \sqrt{1 - \frac{1}{N}} \sigma_u \xrightarrow{N \gg 1} \sqrt{2^B - 1} \sigma_u$$

Generally (X, Y is not excluded)

$$\sigma_{DNL,k} = \sqrt{\text{int}(\text{bin}(k) \oplus \text{bin}(k-1))} \sqrt{1 - \frac{1}{N}} \sigma_u$$

σ_{DNL} (4-bit Example)

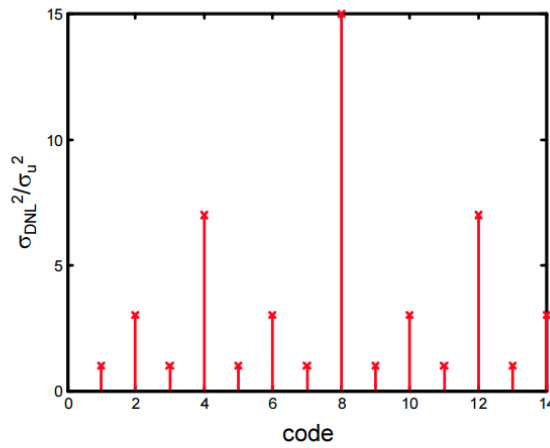

3.1 INL of Segmented DAC

Same as in thermometer DAC

3.2 DNL of Segmented DAC

- Worst case occurs when LSB DAC turns off and one more MSB DAC element turns on
- Essentially same DNL as a binary weighted DAC with B_b+1 bits

$$B = B_t + B_b, B_t=2 \quad B_b=4$$



4 DAC INL/DNL Summary


Comparison

	Thermometer	Segmented	Binary Weighted
σ_{INL} (worst case)	$\cong \frac{1}{2} \sigma_u \sqrt{2^B}$		
σ_{DNL} (worst case)	$\cong \sigma_u$	$\cong \sigma_u \sqrt{2^{B_b+1} - 1}$	$\cong \sigma_u \sqrt{2^B - 1}$
Number of Switched Elements	$2^B - 1$	$B_b + 2^{B_t} - 1$	B

- DAC choice of architecture has significant impact on DNL
- INL is independent of DAC architecture and requires element matching commensurate with overall DAC precision
- Results assume uncorrelated random element variations
- Systematic errors and correlations are usually also important and may affect final DAC performance

Ref. Kuboki, S.; Kato, K.; Miyakawa, N.; Matsubara, K. Nonlinearity analysis of resistor string A/D converters. IEEE Transactions on Circuits and Systems, vol.CAS-29, (no.6), June 1982. p.383-9.

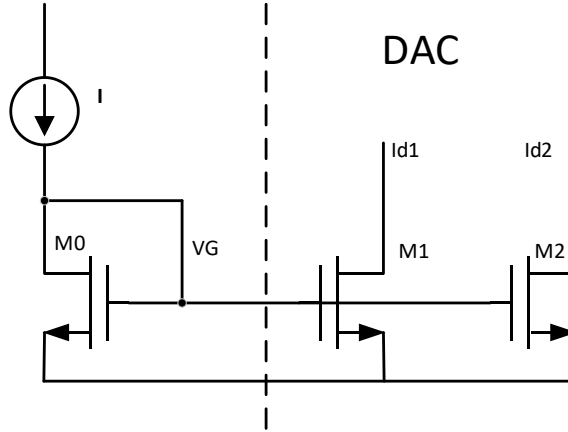5 Demystifying current source variation effect



Since I is forced by external constant current, V_G track the change of $V_{th,0}$, so

$$I_{D1} - I = g_m(\Delta V_{th,0} - \Delta V_{th,1}) - 0$$

$$\frac{\Delta I_{D1,0}}{I} = \frac{g_m}{I}(\Delta V_{th,0} - \Delta V_{th,1}) \xrightarrow{\text{yields}}$$

$$\sigma_{\frac{\Delta I_{D1,0}}{I}} = \frac{g_m}{I} \sqrt{2} \frac{A_{VT}}{\sqrt{2}\sqrt{WL}} = \frac{g_m}{I} \frac{A_{VT}}{\sqrt{WL}}$$

For M1, M2, same $\Delta V_{th,0}$ is applied

$$I_{D2} - I_{D1} = g_m(\Delta V_{th,0} - \Delta V_{th,1}) - g_m(\Delta V_{th,0} - \Delta V_{th,2})$$

$$\Delta I_{D1,2} = g_m(\Delta V_{th,2} - \Delta V_{th,1})$$

$$\frac{\Delta I_{D1,2}}{I} = \frac{g_m}{I}(\Delta V_{th,2} - \Delta V_{th,1}) \xrightarrow{\text{yields}}$$

$$\sigma_{\frac{\Delta I_{D1,2}}{I}} = \frac{g_m}{I} \frac{A_{VT}}{\sqrt{WL}}$$

For DAC part (right side of split line), V_G is fixed, all branches are connected with same voltage level (ΔI_{root} due to M0 variation, $\Delta I_{Dj,self}$ due to M1/2 self-variation)

$$\begin{cases} \Delta I_{D1,tot} = \Delta I_{root} + \Delta I_{D1,self} \\ \Delta I_{D2,tot} = \Delta I_{root} + \Delta I_{D2,self} \end{cases}$$

$$\frac{\Delta I_{D1,tot}}{I} = \frac{\Delta I_{root}}{I} + \frac{\Delta I_{D1,self}}{I} \xrightarrow{\text{yields}} \text{Var}\left(\frac{\Delta I_{D1,tot}}{I}\right) = 2\sigma_u^2$$

$$\sigma_{\frac{\Delta I_{D1,tot}}{I}} = \sqrt{2}\sigma_u = \sqrt{2} \frac{g_m}{I} \frac{A_{VT}}{\sqrt{2}\sqrt{WL}} = \frac{g_m}{I} \frac{A_{VT}}{\sqrt{WL}}$$

Same with $\Delta I_{D2,tot}$


One question, how to get σ_u , subtraction of $\Delta I_{D1,tot}$ and $\Delta I_{D2,tot}$ can filter ΔI_{root} due to current source variation.

$$\Delta I_{D1,tot} - \Delta I_{D2,tot} = \Delta I_{D1,self} - \Delta I_{D2,self} \xrightarrow{\text{yields}} \sigma_{\frac{\Delta I_{D1,2,tot}}{I}} = \sqrt{2} \frac{g_m}{I} \frac{A_{VT}}{\sqrt{2}\sqrt{WL}}$$

Then

$$\sigma_u = \frac{g_m}{I} \frac{A_{VT}}{\sqrt{2}\sqrt{WL}} = \frac{\sigma_{\frac{\Delta I_{D1,2,tot}}{I}}}{\sqrt{2}}$$

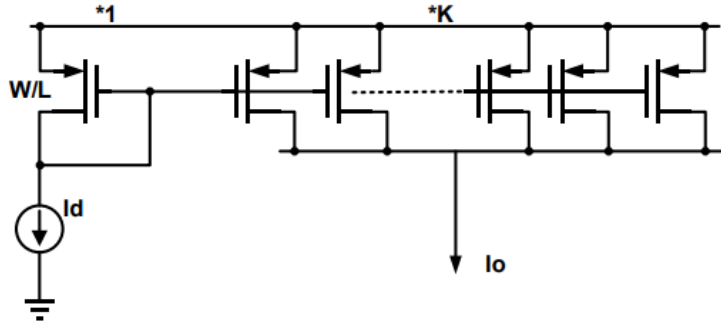6 Current mirror mismatch analysis – another method



$$\Delta I_o = k \cdot \Delta I_{root} + \sum_j^k \Delta I_{Dj,self} \xrightarrow{yields}$$


$$\frac{\Delta I_o}{I_o} = \frac{\Delta I_{root}}{I} + \frac{1}{k} \sum_j^k \frac{\Delta I_{Dj,self}}{I} \xrightarrow{yields}$$

$$Var\left(\frac{\Delta I_o}{I_o}\right) = Var\left(\frac{\Delta I_{root}}{I}\right) + \frac{1}{k^2} Var\left(\sum_j^k \frac{\Delta I_{Dj,self}}{I}\right) \xrightarrow{yields}$$

$$\sigma_{\frac{\Delta I_o}{I_o}} = \sqrt{\sigma_u^2 + \frac{1}{k^2} \cdot k \sigma_u^2} = \sqrt{1 + \frac{1}{k} \sigma_u} = \sqrt{1 + \frac{1}{k} \frac{g_m}{I} \frac{A_{VT}}{\sqrt{2} \sqrt{WL}}}$$

7 practical example – IDAC

Thermometer: 5 bit; Binary: 2 bit

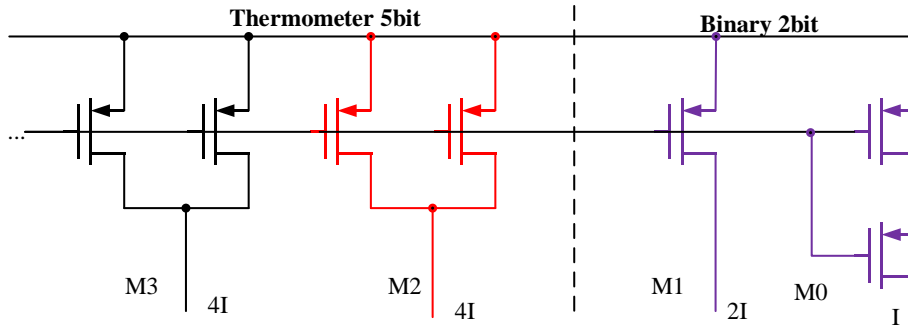

$$stdev\left(\frac{\Delta I}{I}\right) \propto \frac{1}{\sqrt{WL}}$$

$$\begin{cases} stdev\left(\frac{\Delta I_2}{I_2}\right) = \frac{A}{\sqrt{2W \cdot L}} \stackrel{\text{def}}{=} \sigma_u \\ stdev\left(\frac{\Delta I_1}{I_1}\right) = \frac{A}{\sqrt{W \cdot L}} = \sqrt{2} \sigma_u \\ stdev\left(\frac{\Delta I_0}{I_0}\right) = \frac{A}{\sqrt{W \cdot 2L}} = \sigma_u \end{cases}$$

@worst case

$$Var\left(\frac{\Delta I_2 - \Delta I_1 - \Delta I_0}{I}\right) = Var\left(4\frac{\Delta I_2}{4I}\right) + Var\left(2\frac{\Delta I_1}{2I}\right) + Var\left(\frac{\Delta I_0}{I}\right)$$

$$Var\left(\frac{\Delta I_2 - \Delta I_1 - \Delta I_0}{I}\right) = 16\sigma_u^2 + 4 \cdot 2\sigma_u^2 + \sigma_u^2$$


$$stdev\left(\frac{\Delta I_2 - \Delta I_1 - \Delta I_0}{I}\right) = 5\sigma_u \xrightarrow{yields} stdev(DNL) = 5\sigma_u$$

The current difference of 2 thermometer is $\sigma_{\Delta I}$ and equal $\sqrt{2}\sigma_u$

Simulation result $3\sigma_{\Delta I}=110m$, then $3stdev(DNL)=0.389$ LSB

8 practical example – VDAC

Thermometer: 5 bit; Binary: 3 bit

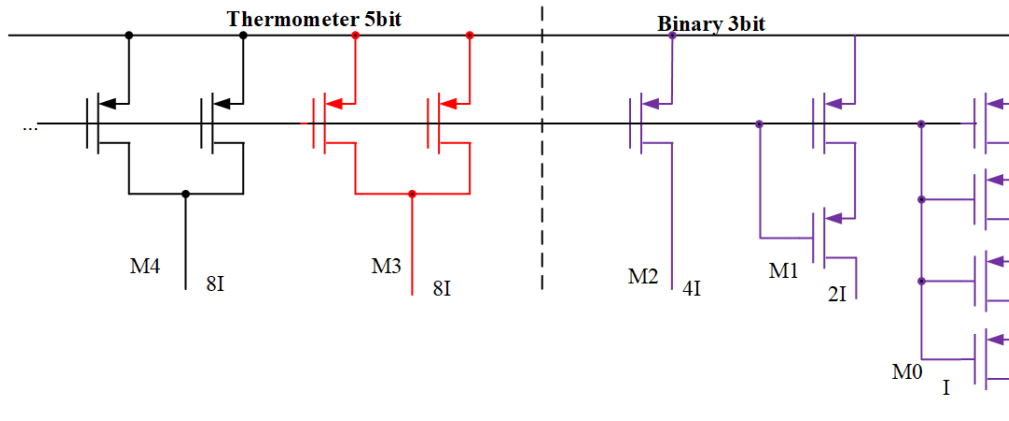

$$\begin{cases} stdev\left(\frac{\Delta I_3}{I_3}\right) = \frac{A}{\sqrt{2W \cdot L}} \stackrel{def}{=} \sigma_u \\ stdev\left(\frac{\Delta I_2}{I_2}\right) = \frac{A}{\sqrt{W \cdot L}} = \sqrt{2}\sigma_u \\ stdev\left(\frac{\Delta I_1}{I_1}\right) = \frac{A}{\sqrt{W \cdot 2L}} = \sigma_u \\ stdev\left(\frac{\Delta I_0}{I_0}\right) = \frac{A}{\sqrt{W \cdot 4L}} = \frac{\sigma_u}{\sqrt{2}} \end{cases}$$

@worst case

$$Var\left(\frac{\Delta I_3 - \Delta I_2 - \Delta I_1 - \Delta I_0}{I}\right) = Var\left(8\frac{\Delta I_3}{8I}\right) + Var\left(4\frac{\Delta I_2}{4I}\right) + Var\left(2\frac{\Delta I_1}{2I}\right) + Var\left(\frac{\Delta I_0}{I}\right)$$

$$Var\left(\frac{\Delta I_3 - \Delta I_2 - \Delta I_1 - \Delta I_0}{I}\right) = 64\sigma_u^2 + 16 \cdot 2\sigma_u^2 + 4\sigma_u^2 + \frac{\sigma_u^2}{2} = 100.5 \cdot \sigma_u^2$$

$$stdev\left(\frac{\Delta I_3 - \Delta I_2 - \Delta I_1 - \Delta I_0}{I}\right) \approx 10\sigma_u \xrightarrow{yields} stdev(DNL) = 10\sigma_u$$

The current difference of 2 thermometer is $\sigma_{\Delta I}$ and equal $\sqrt{2}\sigma_u$

Simulation result $3\sigma_{\Delta I}=35m$, then $3stdev(DNL)=0.247$ LSB

Reference:

ee315b_reader_2013.pdf B. Murmann

Mixed Analog and Digital Integrated Circuit Design 李强/黄乐年 2009–2010 学年下学期